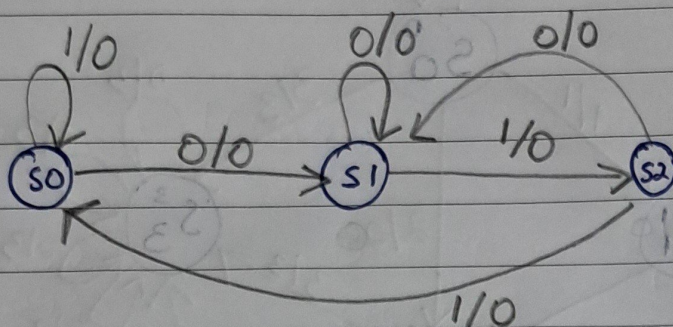


FSM_s - Assignment

- 1.) Draw the state diagram for a FSM, the output toggles whenever it detects '110' LSB first (overlapping). Consider initial value of output as '0'.

= State diagram



Previous State	input	Next State	output(y)
q_1 q_0 I	D_1 D_0	y	
S_0 {	0 0 0	0 1	0
	0 0 1	0 0	0
S_1 {	0 1 0	0 1	0
	0 1 1	1 0	0
S_2 {	1 0 0	0 1	0
	1 0 1	0 0	1
X X X	X X X	0	
X X X	X X X	1	

$D_1 =$

q_1	q_0	I	
0	0	0	1
1	0	0	X

$D_0 =$


q_1	q_0	I	
0	1	0	1
1	0	X	X

$$\therefore D_1 = q_0 I$$

$$D_0 = \bar{I}$$

$$y = q_1 \bar{q}_0 I$$

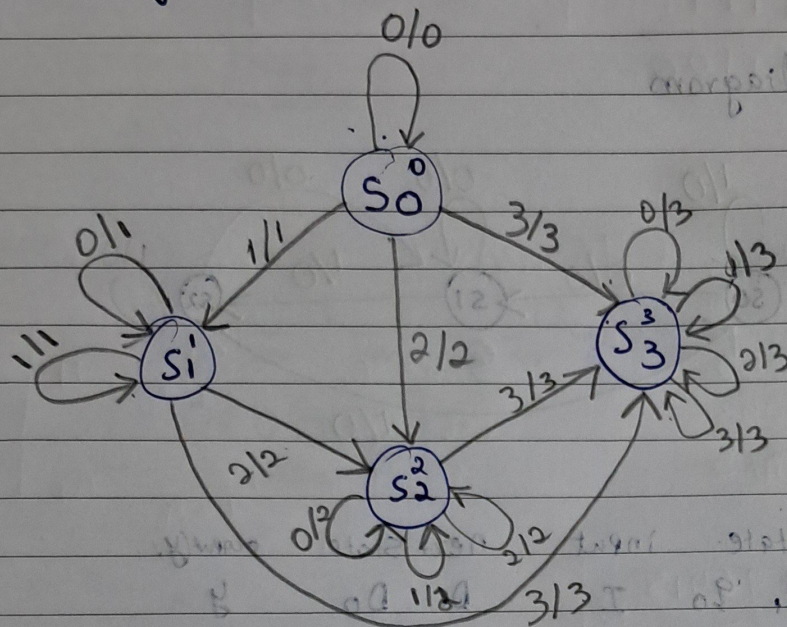2. Design a FSM over $\{0, 1, 2, 3\}$ that will output the largest input digit read so far. eg. input: 001032 will produce output: 001133
- = state diagram.



Previous State	Input	nextstate.
S ₀	0	S ₀
S ₀	1	S ₁
S ₀	2	S ₂
S ₀	3	S ₃
S ₁	0	S ₁ ×
S ₁	1	S ₁ ×
S ₁	2	S ₂
S ₁	3	S ₃
S ₂	0	S ₂
S ₂	1	S ₂
S ₂	2	S ₂
S ₂	3	S ₃
S ₃	0	S ₃
S ₃	1	S ₃
S ₃	2	S ₃
S ₃	3	S ₃