

Registers & Counters- Assignment

1. Design a counter with T flipflops whose count sequence is 0,2,4,5,3,1,0....
2. Design a 3 bit up/down counter using negative edge triggered T-FF.
3. The circuit in the figure below is a counter. What is the sequence that this circuit counts in?

